



CUMIN - MOUVE

<https://cumin.univ-lille.fr/>

Study of a bidirectional onboard power charger



Authors : Fadwa BENFYALA
Mohamed BENIDAR
Mohamed BOUTSOUDINE

Supervisor : Mr. Philippe Delarue

Affiliation(s) : Université de Lille

Outline

1

Context and objective

2

Literature review

3

Our case study

4



Conclusion and perspectives




<https://cumin.univ-lille.fr/>

Context and objective

Context and objective

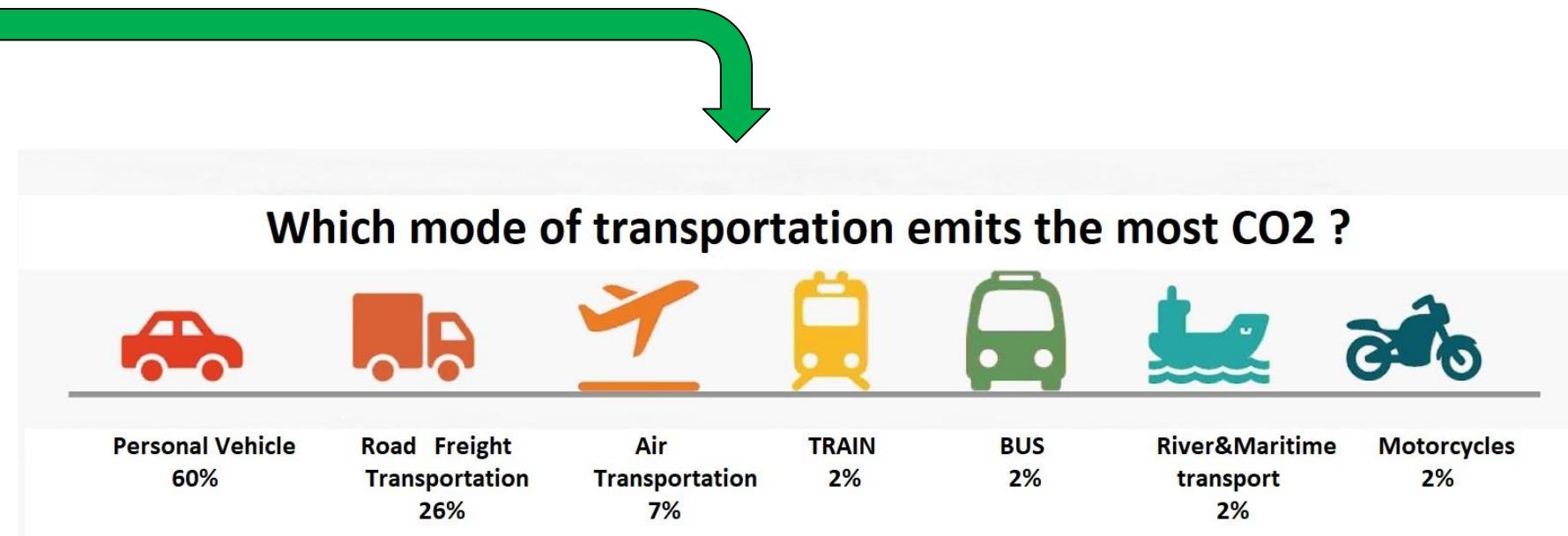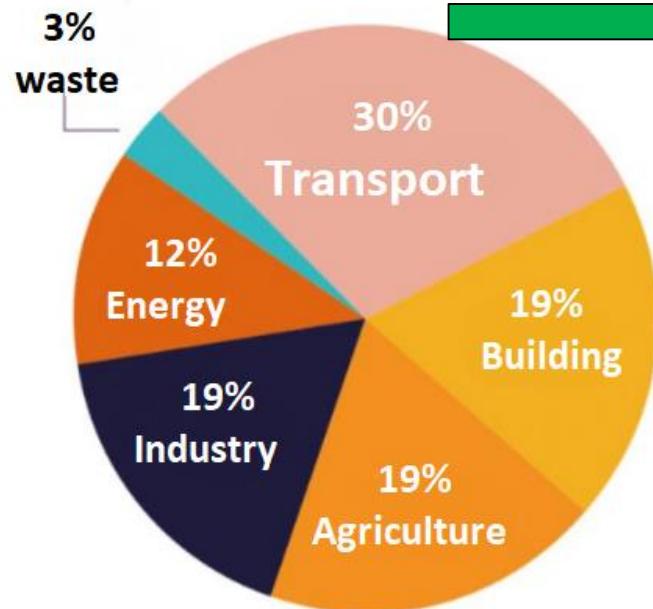

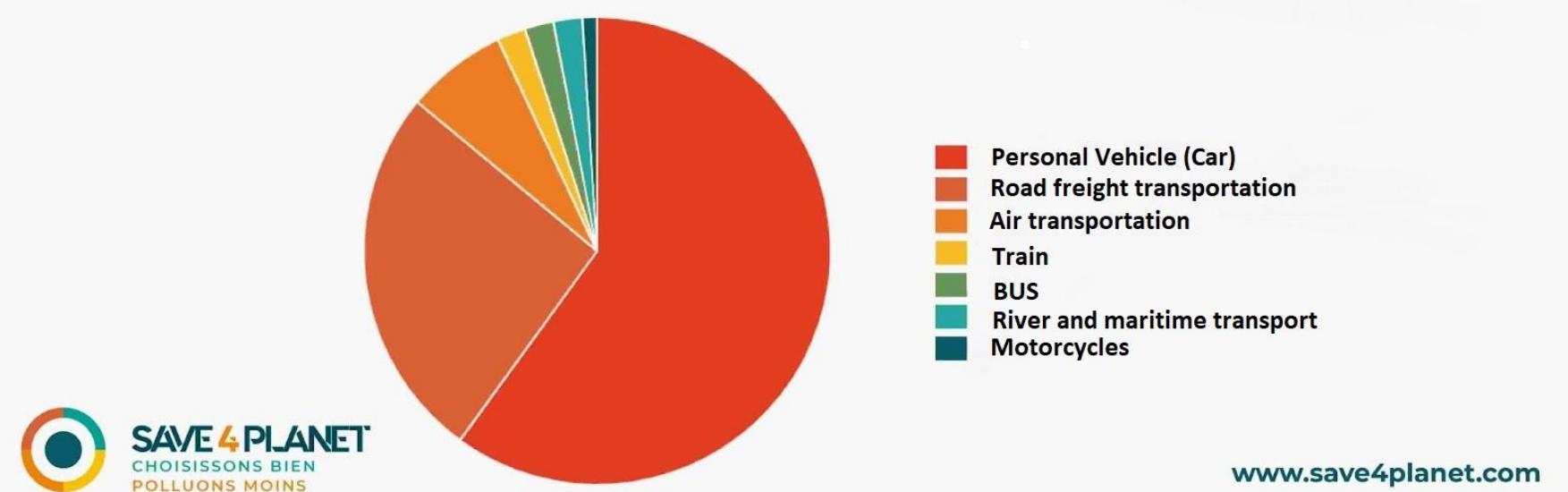Greenhouse Gas Emissions sectoral distribution in France in 2019



Context and objective


Positioning in the CUMIN programme

Campus of University with Mobility based on Innovation and carbon Neutral



Our project : **CUMIN MOUVE**

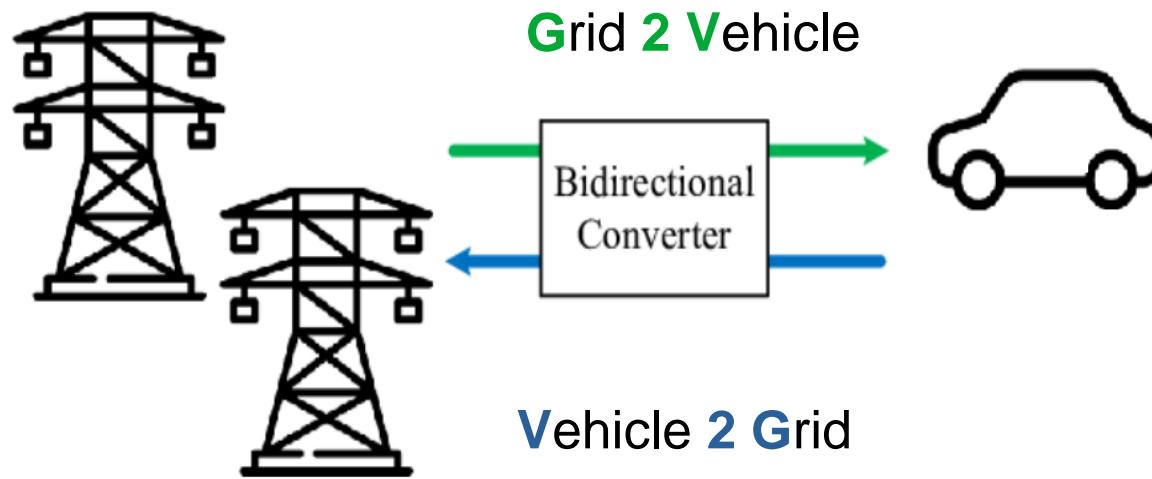MOUVE : MObility and USE of electric VEhicles based on dedicated charging infrastructure



Objective : Determining the control of a bidirectional onboard power charger




<https://cumin.univ-lille.fr/>

Literature review

Literature review

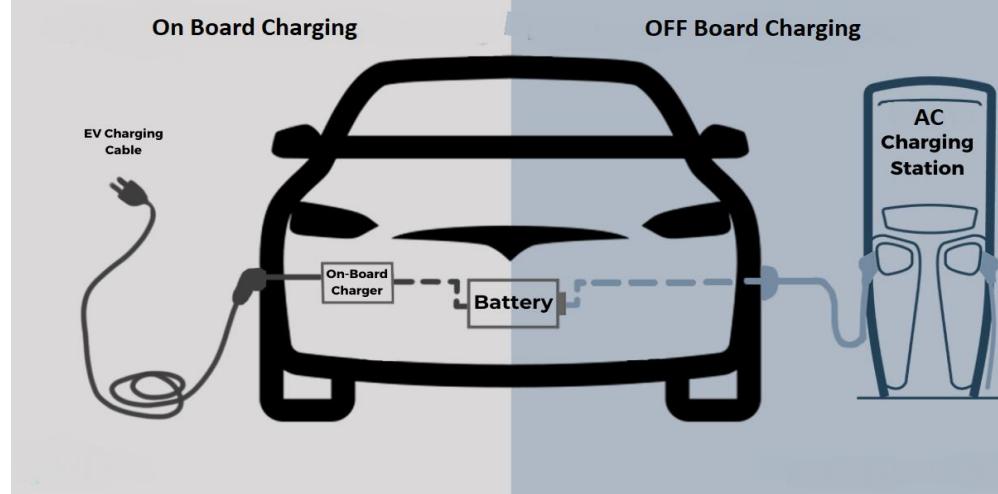Currently, there are two types of chargers...



Literature review

Why should we use a bidirectional OBC instead of classic charger ?




V2H (Vehicle To Home)




V2L (Vehicle To Load)

Bidirectional
OBC

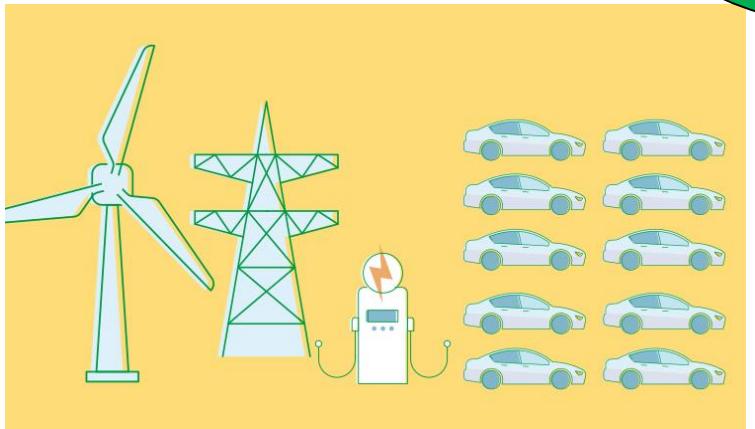

V2G (Vehicle To Grid)

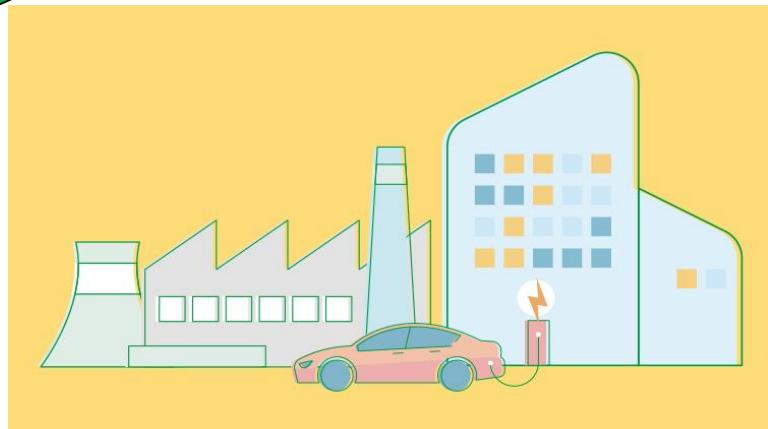

V2X (Vehicle To Everything)



<https://cumin.univ-lille.fr/>

Our case study

Our case study


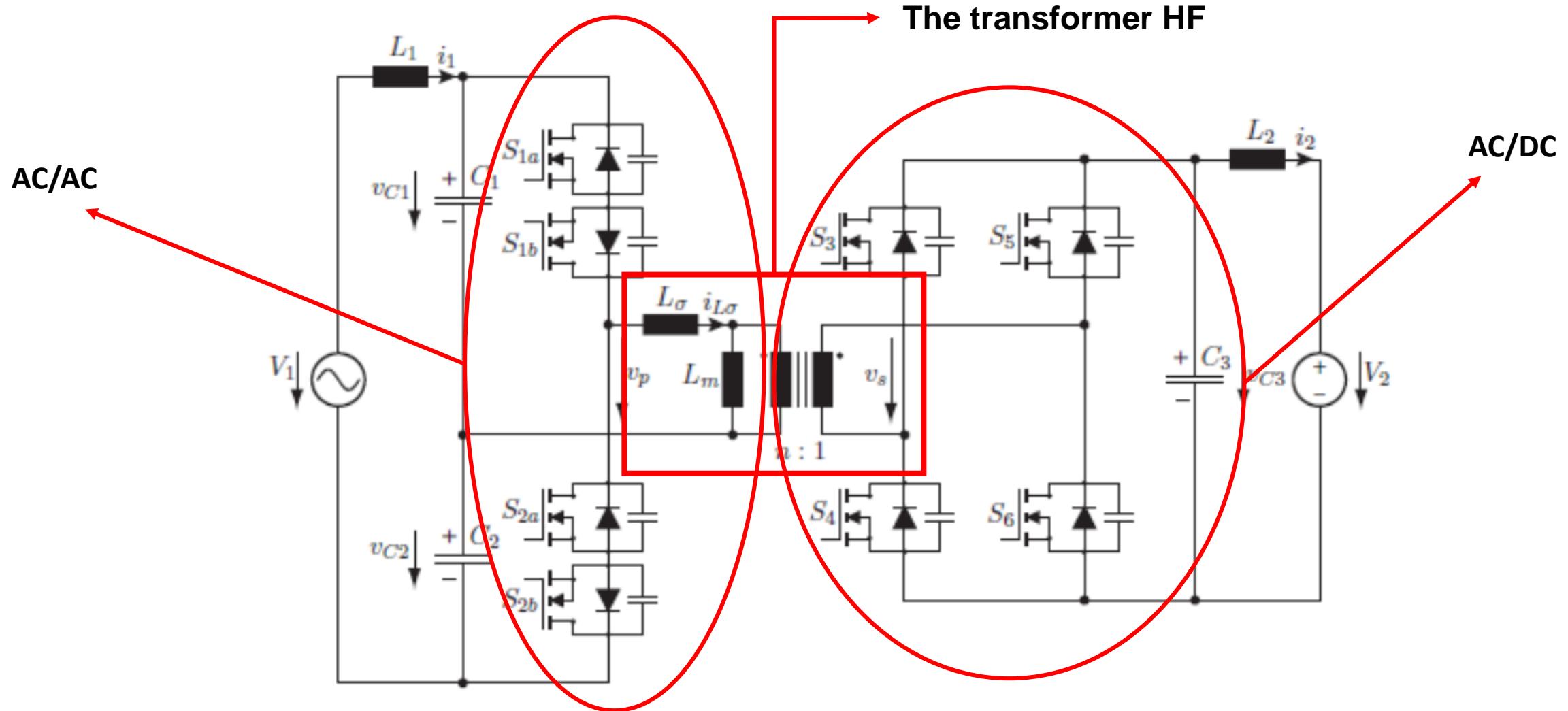


Figure : F. Jauch, J. Biela « Single-Phase Single-Stage Bidirectional Isolated ZVS AC-DC Converter with PFC »


Our case study

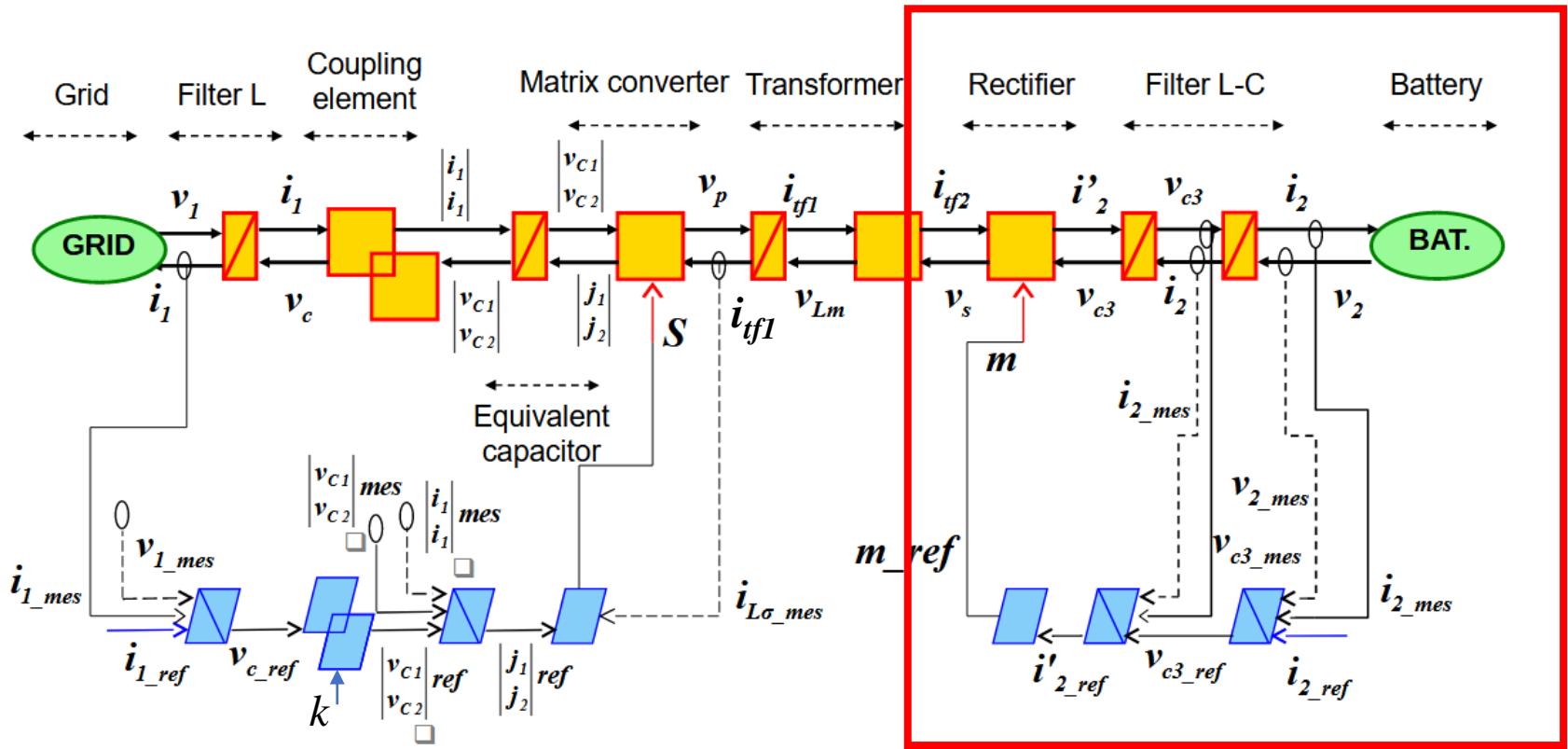

Model and control structure by EMR

EMR : Energetic Macroscopic Representation

Simulation Tools

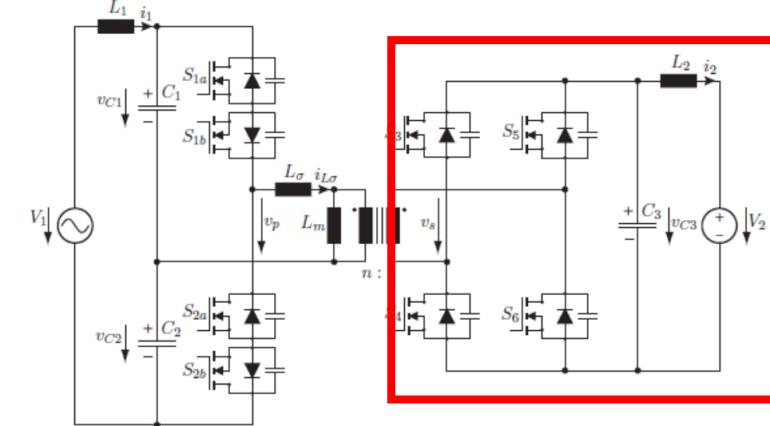

Objective : Determine the control of a bidirectional onboard power charger

Our case study

Grid 2 Vehicle


- Battery charging : Positif current
- Rectifier : AC/DC conversion

Vehicle 2 Grid

- Battery discharging : Negatif current
- Rectifier : Become an inverter

Objective :

Control of the battery current i_2

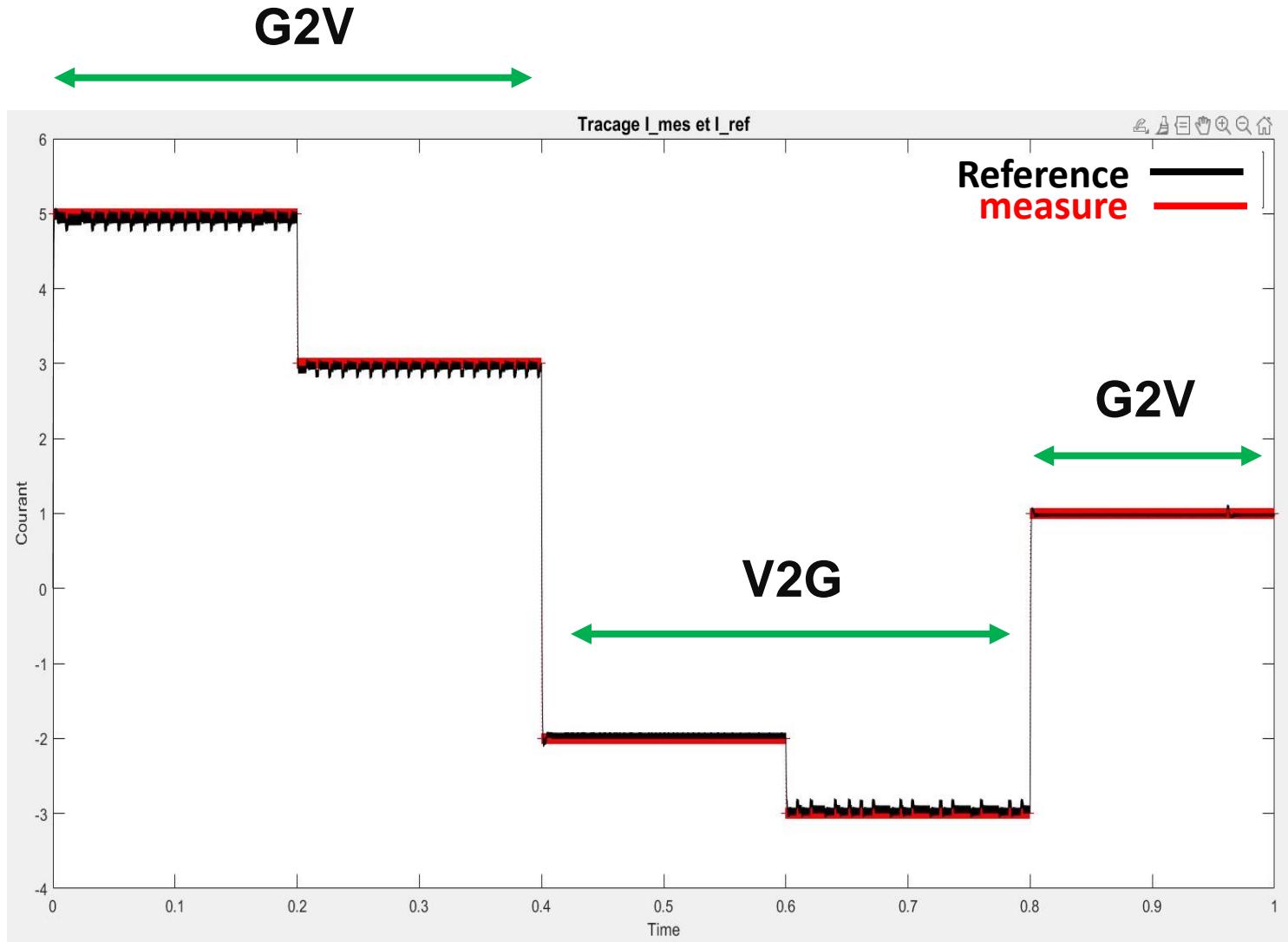

Evolution of the battery current





<https://cumin.univ-lille.fr/>

Conclusion and perspectives

Conclusion and perspectives

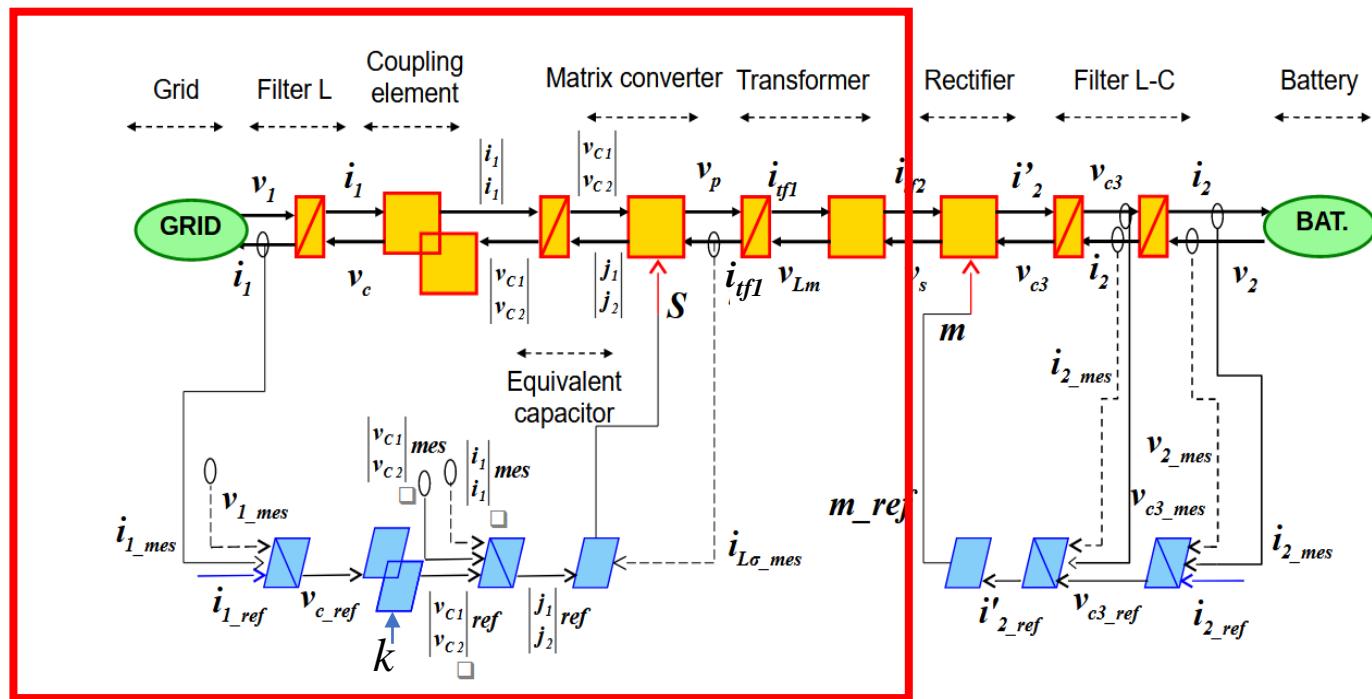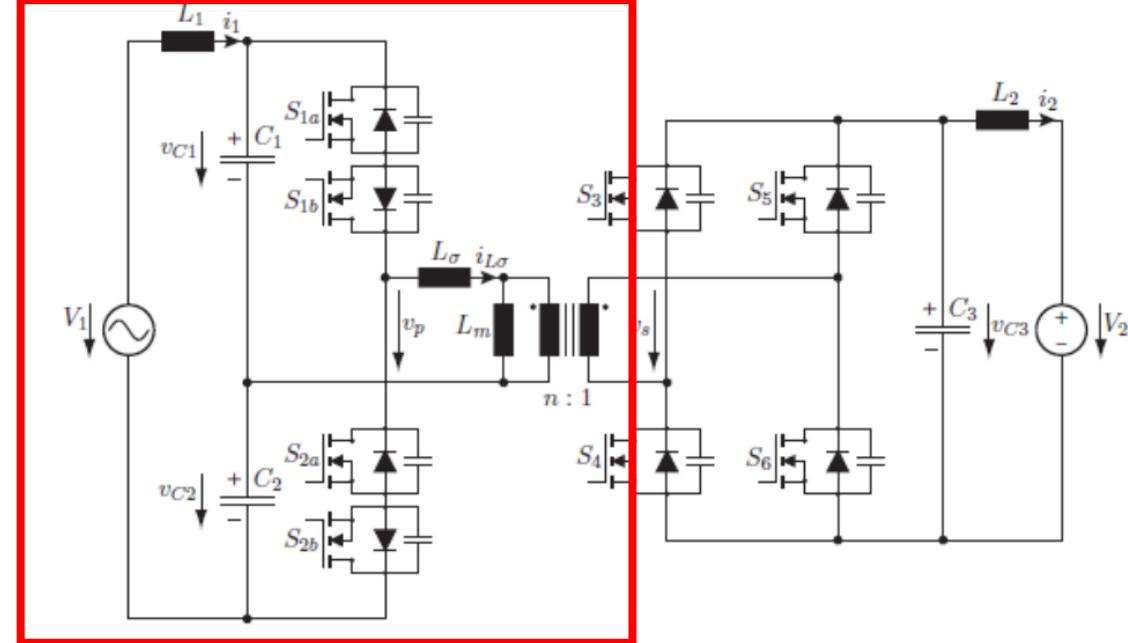- **Objective :** Determine the control of a bidirectional onboard power charger.
- **Step 1 :** Inverting the first subsystem and controlling the battery current i_2
- **Step 2 :** Inverting the second subsystem and controlling the grid current i_1
- **Step 3 :** Combine the two subsystems





<https://cumin.univ-lille.fr/>

Annexe


Annexe

The different structures of a bidirectional onboard power charger

Structure of a charger **without a transformer**




Single stage

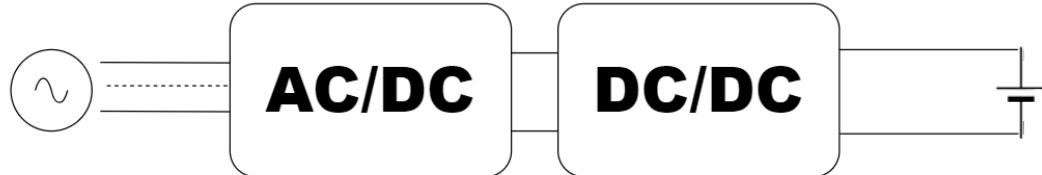


Two stage

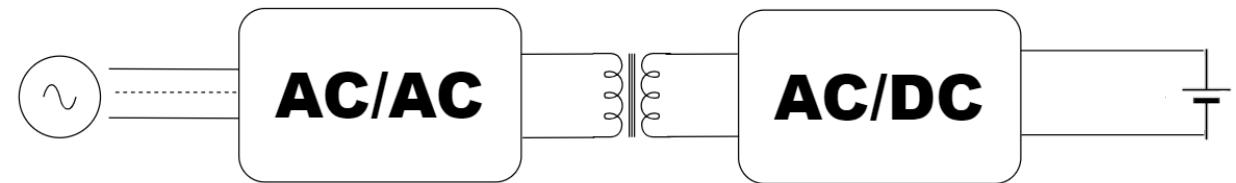Structure of a charger **with a transformer**




Single stage

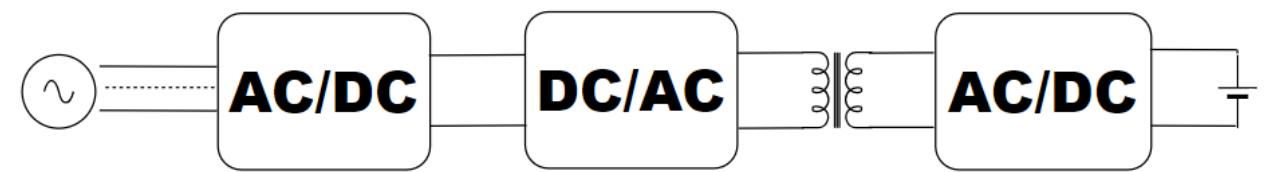


Two stage

Annexe

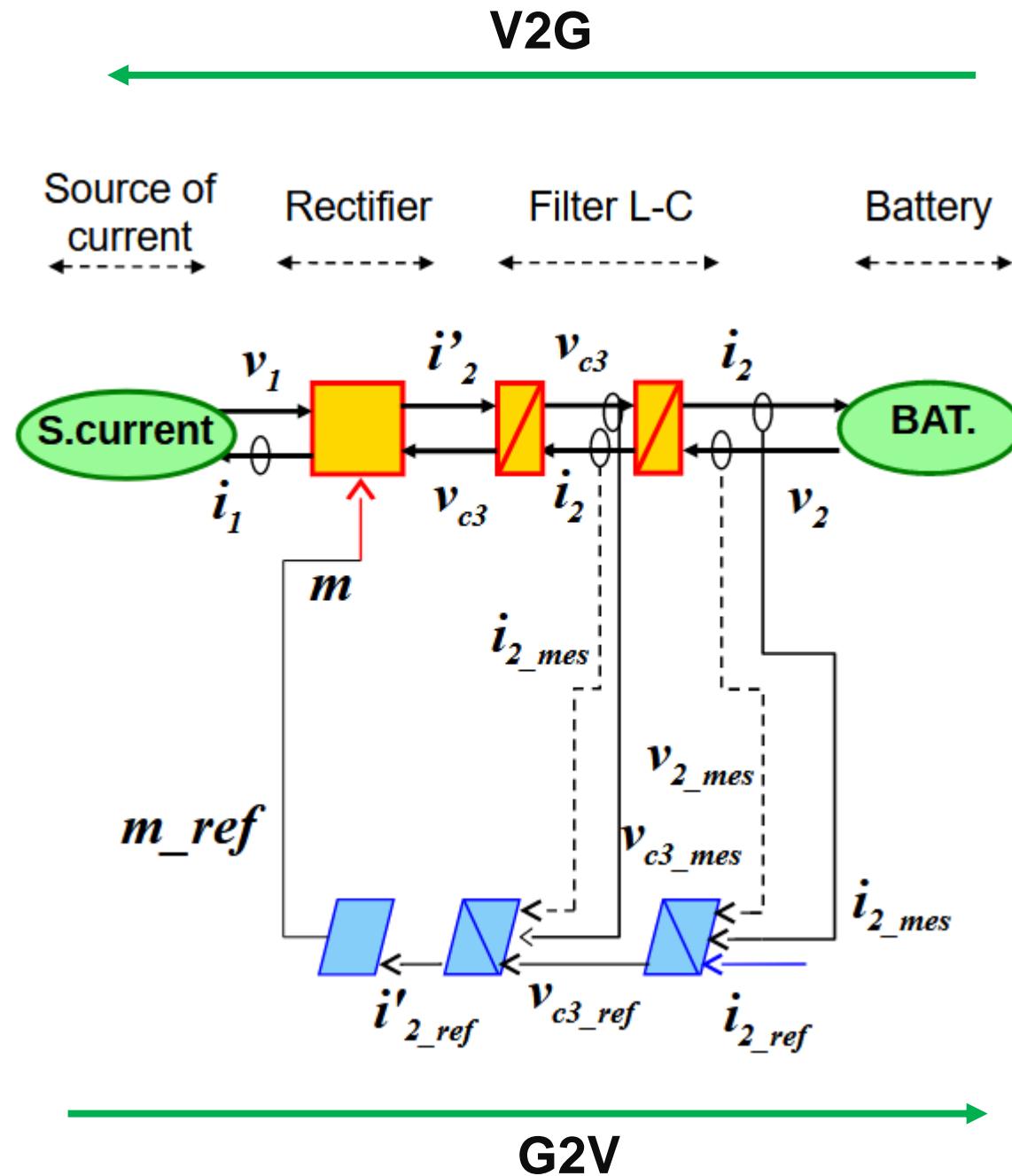



Annexe

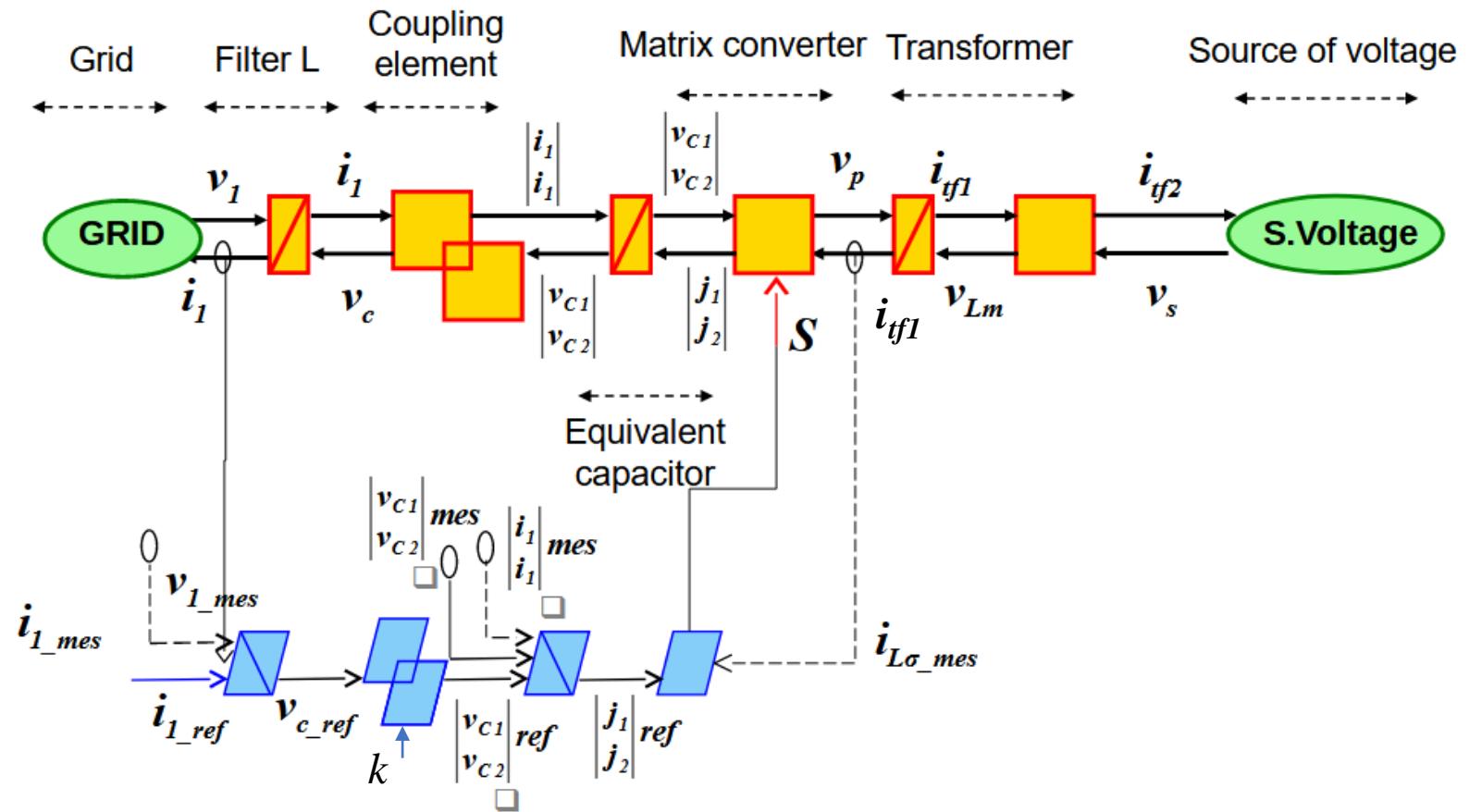

Objective : Control of the grid current i_1



<https://cumin.univ-lille.fr/>

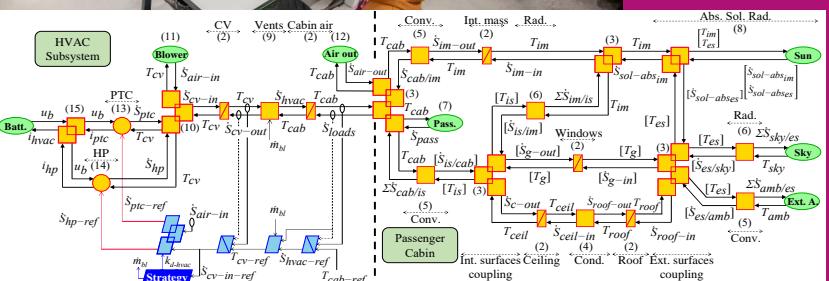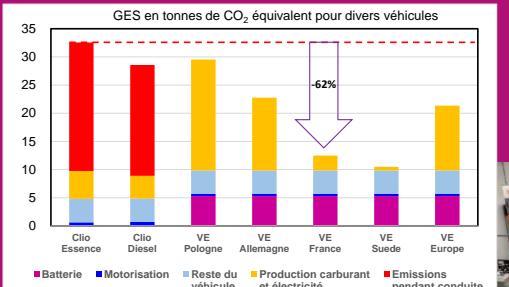

Our university as
an exciting living lab
towards eco-cities
through an innovative
transdisciplinary
framework !

